

Laboratórna úloha číslo 2

Autor : Daniel Haluška ID:220816 <https://github.com/DaNNym99/Digital-electronics-1>

1. Pravdivostná tabuľka:

Dec. equivalent	B[1:0]	A[1:0]	B > A	B = A	B < A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1
3	0 0	1 1	0	0	1
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0

1.1. Funkcie B=A a B<A:

$$eqals_{SoP} = (\overline{A_0} \cdot \overline{A_1} \cdot \overline{B_0} \cdot \overline{B_1}) + (A_0 \cdot \overline{A_1} \cdot B_0 \cdot \overline{B_1}) + (\overline{A_0} \cdot A_1 \cdot \overline{B_0} \cdot B_1) + (A_0 \cdot A_1 \cdot B_0 \cdot B_1)$$

$$less_{PoS} = (A_0 + A_1 + B_0 + B_1) \cdot (A_0 + A_1 + \overline{B_0} + B_1) \cdot (\overline{A_0} + A_1 + \overline{B_0} + B_1) \cdot (A_0 + A_1 + B_0 + \overline{B_1}) \cdot (\overline{A_0} + A_1 + B_0 + \overline{B_1}) \cdot (A_0 + \overline{A_1} + B_0 + \overline{B_1}) \cdot (A_0 + A_1 + \overline{B_0} + \overline{B_1}) \cdot (\overline{A_0} + A_1 + \overline{B_0} + \overline{B_1}) \cdot (A_0 + \overline{A_1} + \overline{B_0} + \overline{B_1}) \cdot (\overline{A_0} + \overline{A_1} + \overline{B_0} + \overline{B_1})$$

2. Karnaughove mapy

B > A

		A1 A0			
		00	01	11	10
B1 B0	00				
	01	1			
	11	1	1		1
	10	1	1		

2.1. Zjednodušená forma SoP B>A funkcie

$$great\ SoP = (B_1 \cdot \overline{A_1}) + (\overline{A_0} \cdot \overline{A_1} \cdot B_0) + (\overline{A_0} \cdot B_0 \cdot B_1)$$

B = A

		A1 A0			
		00	01	11	10
B1 B0	00	1			
	01		1		
	11			1	
	10				1

B < A


		A1 A0			
		00	01	11	10
B1 B0	00	0			
	01	0	0		
	11	0	0	0	0
	10	0	0		0

2.2. Zjednodušená forma PoS B < A funkcie

$$less\ PoS = (A_0 + A_1) \cdot (A_1 + \overline{B_0}) \cdot (\overline{B_0} + \overline{B_1}) \cdot (A_1 + \overline{B_1}) \cdot (A_0 + \overline{B_1})$$

2.3. Link na edaplayground (2-bit komparátor): <https://www.edaplayground.com/x/rnP9>

2.4. Obrázok výstupu

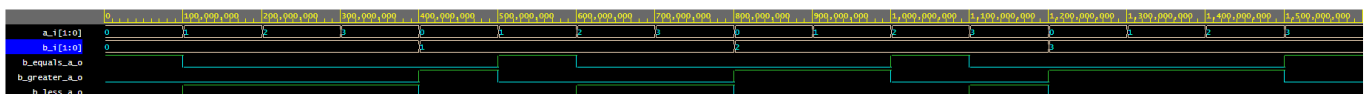

3. Binárny Komparátor 4-bit

3.1. Link na edaplayground (4-bit komparátor): <https://www.edaplayground.com/x/7fe3>

3.2. Súbor design.vhd

```

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for 4-bit binary comparator
-----
entity comparator_2bit is
    port(
        a_i          : in  std_logic_vector(4 - 1 downto 0);
        b_i          : in  std_logic_vector(4 - 1 downto 0);
        B_greater_A_o : out std_logic;      -- B is less than A
        B_equals_A_o  : out std_logic;      -- B is less than A
        B_less_A_o    : out std_logic      -- B is less than A
    );
end entity comparator_2bit;

-----
-- Architecture body for 4-bit binary comparator
-----
architecture Behavioral of comparator_2bit is
begin

    B_greater_A_o <= '1' when (b_i > a_i) else '0';
    B_equals_A_o  <= '1' when (b_i = a_i) else '0';
    B_less_A_o    <= '1' when (b_i < a_i) else '0';

end architecture Behavioral;

```

3.3. Súbor testbench.vhd

```

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_comparator_2bit is
    -- Entity of testbench is always empty
end entity tb_comparator_2bit;

-----
-- Architecture body for testbench
-----
architecture testbench of tb_comparator_2bit is

    -- Local signals
    signal s_a          : std_logic_vector(4 - 1 downto 0);
    signal s_b          : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;

```

```

    signal s_B_less_A      : std_logic;

begin
    -- Connecting testbench signals with comparator
    uut_comparator_2bit : entity work.comparator_2bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o  => s_B_greater_A,
            B_equals_A_o   => s_B_equals_A,
            B_less_A_o     => s_B_less_A
        );

    -----
    -- Data generation process
    -----

    p_stimulus : process
    begin
        -- Report a note at the begining of stimulus process
        report "Stimulus process started" severity note;

        -- Test values
        s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0000" severity error;

        -- Test values
        s_b <= "0001"; s_a <= "0000"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
        -- If false, then report an error
        report "Test failed for input combination: 0001, 0000" severity error;

        -- Test values
        s_b <= "0001"; s_a <= "0010"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
        -- If false, then report an error
        report "Test failed for input combination: 0001, 0010" severity error;

        -- Test values
        s_b <= "0100"; s_a <= "0110"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
        -- If false, then report an error
        report "Test failed for input combination: 0100, 0110" severity error;

        -- Test values

```

```

s_b <= "1111"; s_a <= "1100"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
-- If false, then report an error
report "Test failed for input combination: 1111, 1100" severity error;

-- Test values
s_b <= "0110"; s_a <= "1001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
-- If false, then report an error
report "Test failed for input combination: 0110, 1001" severity error;

-- Test values
s_b <= "0111"; s_a <= "1110"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
-- If false, then report an error
report "Test failed for input combination: 0111, 1110" severity error;

-- Test values
s_b <= "0011"; s_a <= "0011"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
-- If false, then report an error
report "Test failed for input combination: 0011, 0011" severity error;

-- Test values
s_b <= "1000"; s_a <= "0100"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
-- If false, then report an error
report "Test failed for input combination: 1000, 0100" severity error;

-- Test values
s_b <= "1111"; s_a <= "1111"; wait for 100 ns;
-- Expected output with error (s_B_equals_A = '1')
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
-- If false, then report an error
report "Test failed for input combination: 1111, 1111" severity error;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

3.4. Umelo vytvorený error v konzole

```
[2021-02-18 11:17:14 EST] ghdl -i design.vhd testbench.vhd && ghdl -m
tb_comparator_2bit && ghdl -r tb_comparator_2bit --vcd=dump.vcd && sed -i
's/^U/X/g; s/^-/X/g; s/^H/1/g; s/^L/0/g' dump.vcd
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_2bit
testbench.vhd:51:9:@0ms:(report note): Stimulus process started
testbench.vhd:112:9:@1us:(assertion error): Test failed for input combination:
1111, 1111
testbench.vhd:117:9:@1us:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-18 11:17:15 EST] Opening EPWave...
Done
```

3.5. Obrázok výstupu

